

Sait Sarper Özaslan

102-2

7/11/2022

## Lab 4 Report: Arithmetic Logic Unit(ALU)

### Purpose:

The purpose of this lab is to learn how to design an Arithmetic Logic Unit(ALU) that consists of addition, subtraction and 6 more operations which must include at least one bitwise and one bit shift operations.

### Design Specifications and Methodology:

To make the ALU specified I needed 8 different operations to fit into specifications wanted. The ALU I made consists of Addition, Subtractor, Comparator, Rotate Left, Ones complement, NAND gate, OR gate and XOR gate. While Rotate Left is a bit shift operation, the gate operations and Ones Complement are the bit wise operations in the ALU I made. The left-out operations are arithmetic operations. To visualize the connections between operators an RTL schematic should be used, and this schematic can be further supported through a testbench, which lets me see whether the operations are working properly or not.

To be able to specify between these operations I needed a 3-bit multiplexer which means I needed 3 inputs in the BASYS3 to pick between operations. I decided to use two 3-bit numbers to have more variety between the results of operations. Considering the addition operation being able to give a 4-bit number as its' end result, I decided to use a 4-bit number to show output. For each 3-bit input I needed to put 3 inputs as switches to the BASYS3 and as for outputs I needed to use 4 LEDs to display the output appropriately.

For two 3-bit input numbers' inputs I used X1\_in, X2\_in X3\_in and Y1\_in, Y2\_in, Y3\_in. As for multiplexer's inputs I used Mult(0), Mult(1) and Mult(2). Finally for outputs I used Z as a logic vector '3 downto 0 '.

All of the modules are coded in a modular fashion which gets combined into one big module which I named 'Topmod'.

In other words, I first have,

- Topmod.vhdl

Under this module I have:

- Addition.vhdl
- Subtractor.vhdl
- Comparator.vhdl
- Rotateleft.vhdl
- Onescomplement.vhdl
- Nandgate.vhdl
- Orgate.vhdl
- Xorgate.vhdl

To be able to use addition and subtractor module I also needed a half adder and full adder which are put under these 2 modules as:

- Half\_adder.vhdl
- Full\_adder.vhdl

| Operations           | Input Example | Output Example |
|----------------------|---------------|----------------|
| "000" /Summation     | 010 /101      | 0101           |
| "001"/ Subtractor    | 110/ 101      | 0001           |
| "010"/ Comparator    | 101/ 011      | 0010           |
| "011"/RotateLeft     | 101           | 0011           |
| "100"/Onescomplement | 110           | 0001           |
| "101"/Nandgate       | 101/110       | 0011           |
| "110"/Orgate         | 010/100       | 0110           |
| "111"/ Xorgate       | 101/011       | 0110           |

Figure 1.1 Operations

Results:

To begin with, the ALU was designed through VHDL. I designed the sub module half adder and full adder first to be able to do subtraction and summation. As I created each operations'

module I also added these modules to top module I have made so that I can display it's RTL schematic. The RTL schematic of the ALU is:

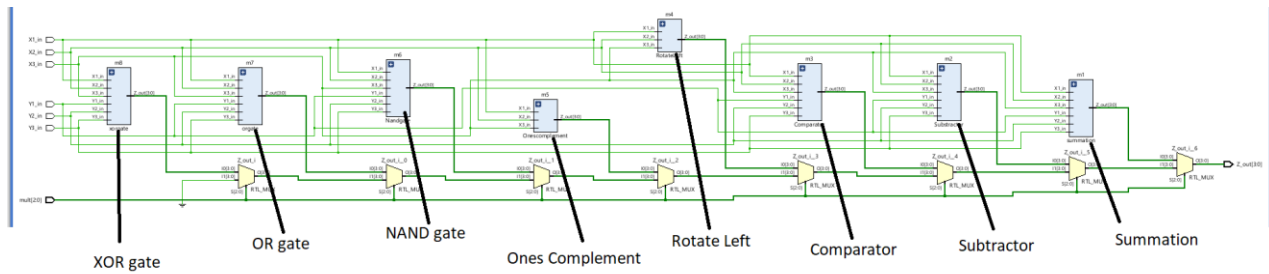


Figure 1.2: The RTL Schematic of ALU

On the simulation there were several options to display, however I only chose 3 of them:

Case 1: I used 111 for 3-bit number for X's inputs and 111 for 3-bit number Y's inputs which can be seen from the figure the results were appropriate to multiplexers results.

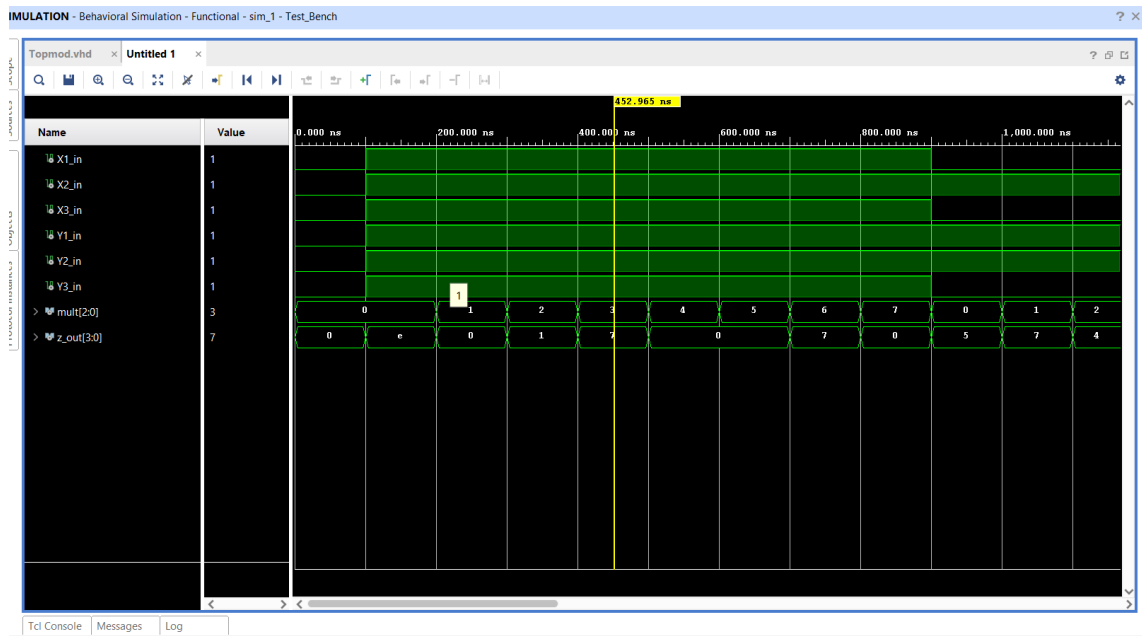


Figure 1.3: Case 111/111

Case 2: I used 010 for X and 111 for Y. There were no undefined values or errors in this part as well.

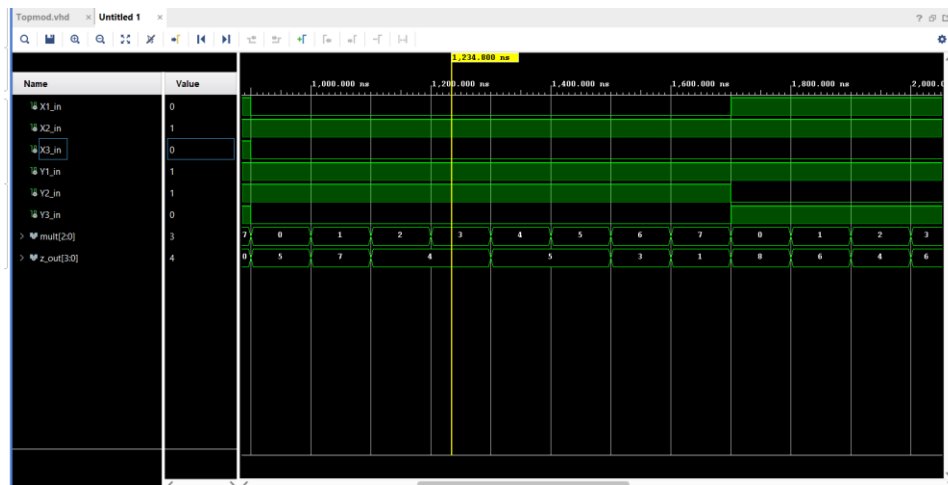


Figure 1.4: Case 010/111

Case 3: I used 011 and 101 for this case. To not get confused I put X3\_in to X1\_in in most significant bit to least significant bit order. Same for Y3\_in to Y1\_in as well.

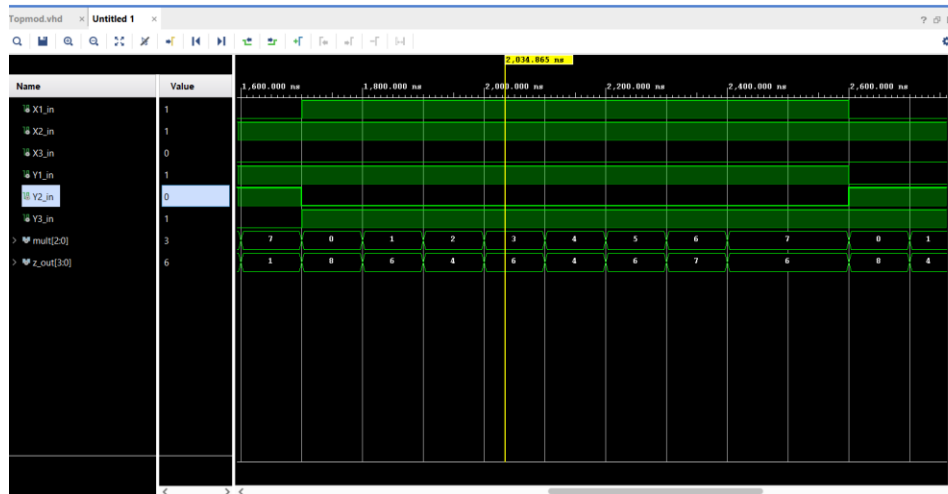


Figure 1.5: Case 011/101

After creating the simulation all there was left is to create the constraint file to implement it into BASYS3. The implementation I used for this lab was:

X1\_in: V17 Switch,

X2\_in: V16 switch,

X3\_in W16 Switch

- I left W 17 switch empty to be able to differentiate easily between inputs

Y1\_in: W15 Switch

Y2\_in: V15 Switch

Y3\_in: W14 Switch

- For multiplexer;

Mult(0) : V1 Switch

Mult(1) : T1 Switch

Mult(2) : R2 Switch

- For Outputs;

Z\_out(0): U16 LED

Z\_out(1): E19 LED

Z\_out(2): U19 LED

Z\_Out(3):V19 LED

 


Figure 1.6 : BASYS3 Configuration

Then I started to test the operations I have written on the BASYS3. Here are all 8 cases and examples for each one of them. I have put small papers in between switches so that the observations can be made easier.

### Summation:

Multiplexer signal: 000

3-bit X Input: 111

3-bit Y Input: 110

Expected Result: 1101

 


Figure 1.7: Case 111/101 on Summation

### Subtractor:

Multiplexer Signal: 001

3-bit X Input: 101

3-bit Y Input: 011

Expected Result: 0010

 


Figure 1.8: Case 101/011 on Subtraction

Comparator:

When Z\_out(2) turns on it is less than, when Z\_out(1) turns on the result is greater than and when Z\_out(0) turns on it is equal.

Multiplexer Signal: 010

3-bit X Input: 101

3-bit Y Input:101

Expected Result:0001

 


Figure 1.9: Case 101/101 on Comparator

Rotate Left



Multiplexer Signal:011

3-bit X Input:101

Expected Result:0011

 


Figure 1.10: Case 101 on Rotate Left

### Ones Complement:

Multiplexer Signal: 101

3-bit X Input: 110

Expected Result:0001

 


Figure 1.11 Case 110 on Ones Complement

NAND Gate

Multiplexer Signal: 101

3-bit X Input:110

3-bit Y Input:010

Expected Result:0101

 


Figure 1.12: Case 110/010 on NAND Gate

OR Gate

Multiplexer Signal:110

3-bit X Input: 110

3-bit Y Input:101

Expected Result:0111

 


Figure 1.13: Case 110/101 on OR Gate

### XOR Gate

Multiplexer Signal:111

3-bit X Input:101

3-bit Y Input:100

Expected Result:0001

 


Figure 1.14: Case 101/100 on XOR Gate

It can be seen from the examples the expected results aligned with the actual results.

### Conclusion:

Throughout this lab, I implemented an ALU into the BASYS3. To implement this ALU I wrote codes for eight operations. One error I had to struggle with was the comparator's VHDL code as I firstly started to write the code through a lengthy Boolean expression. This required me to add several signals to the code making it more confusing. To fix this issue I examined the comparator's gate structure which we had learnt in class and implemented the comparator accordingly. One other issue I faced was with the subtractor as I realized there needs to be two's complement code and a comparator for the cases where 3-bit input Y is bigger than 3-bit X. Otherwise, the subtractor works perfectly fine. Finally, there were no significant errors in testbench which allowed me to observe the behavior of ALU easily.

### Appendix:

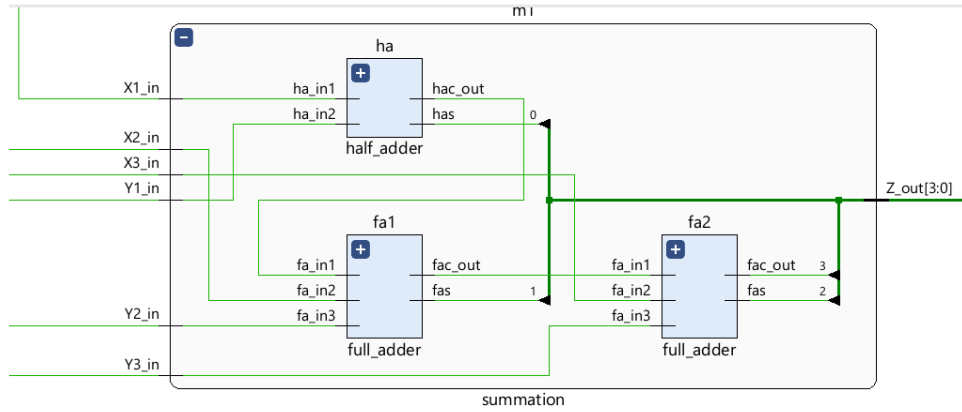


Figure 1.15: RTL Schematic for Summation

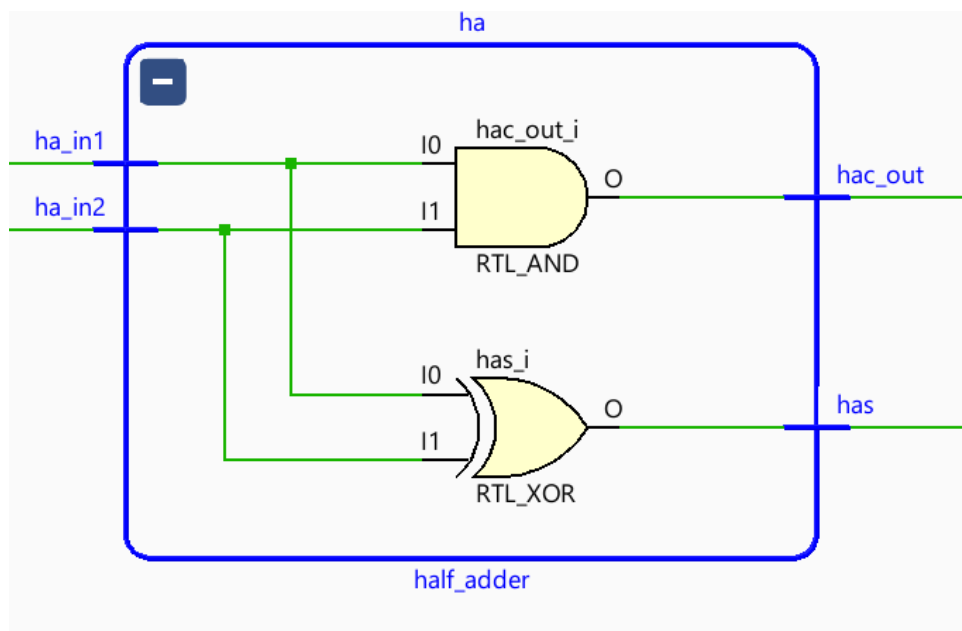


Figure 1.16: RTL Schematic of Half Adder

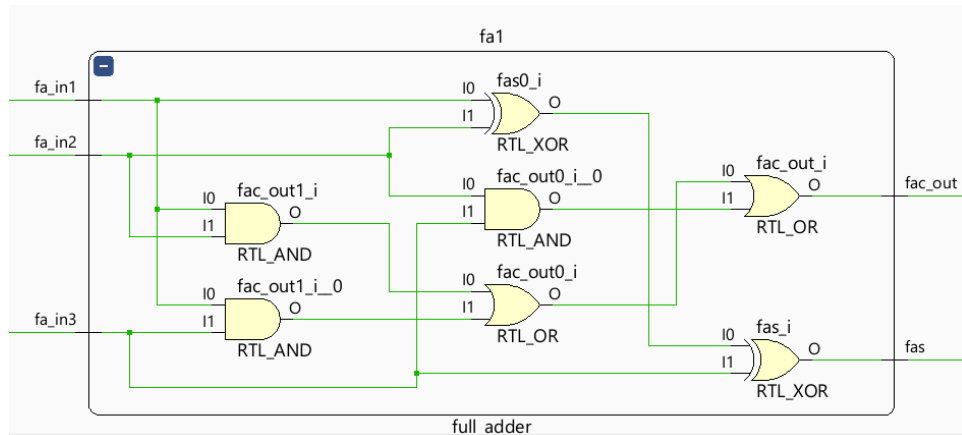


Figure 1.17: RTL Schematic of Full Adder

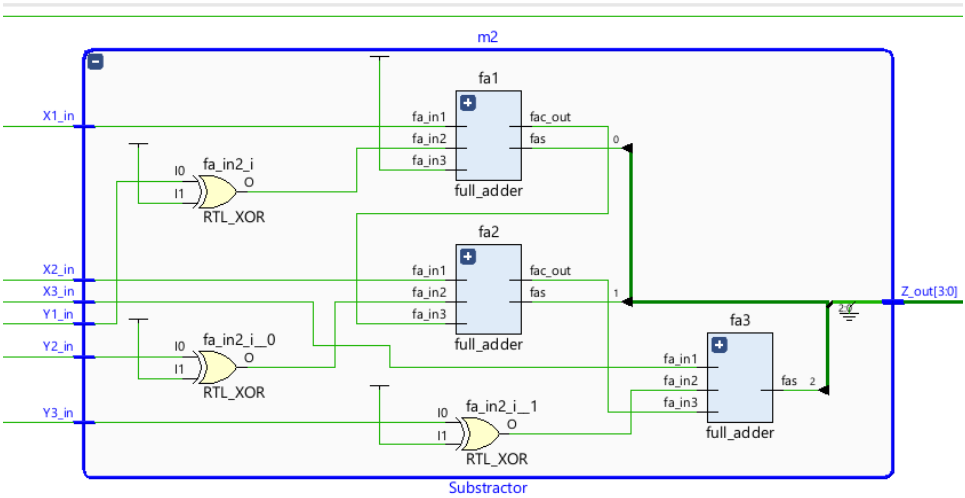


Figure 1.18: RTL Schematic of Subtractor

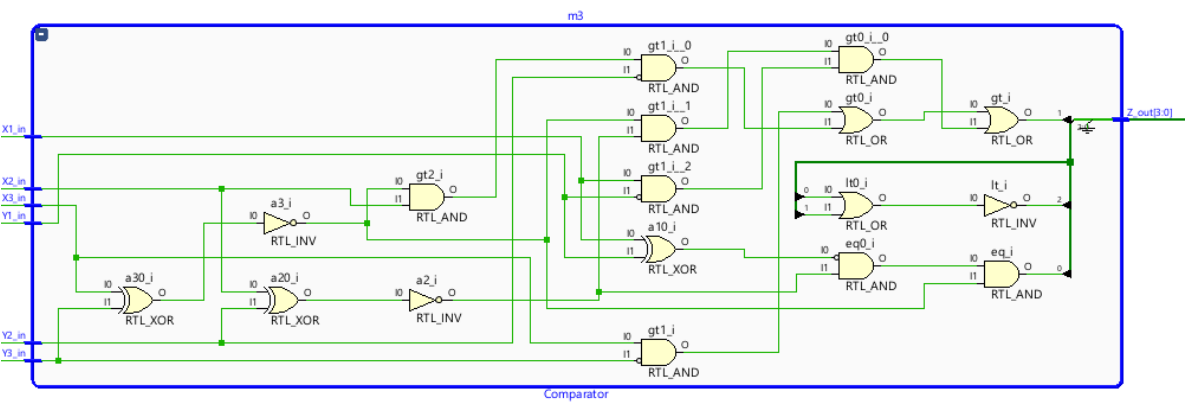


Figure 1.19: RTL Schematic of Comparator

 


Figure 1.20: RTL Schematic of Rotate Left

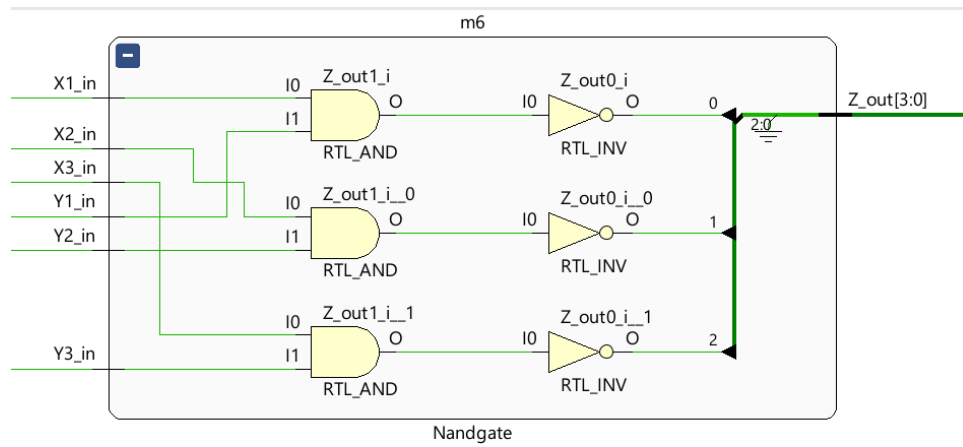


Figure 1.21: RTL Schematic of NAND Gate



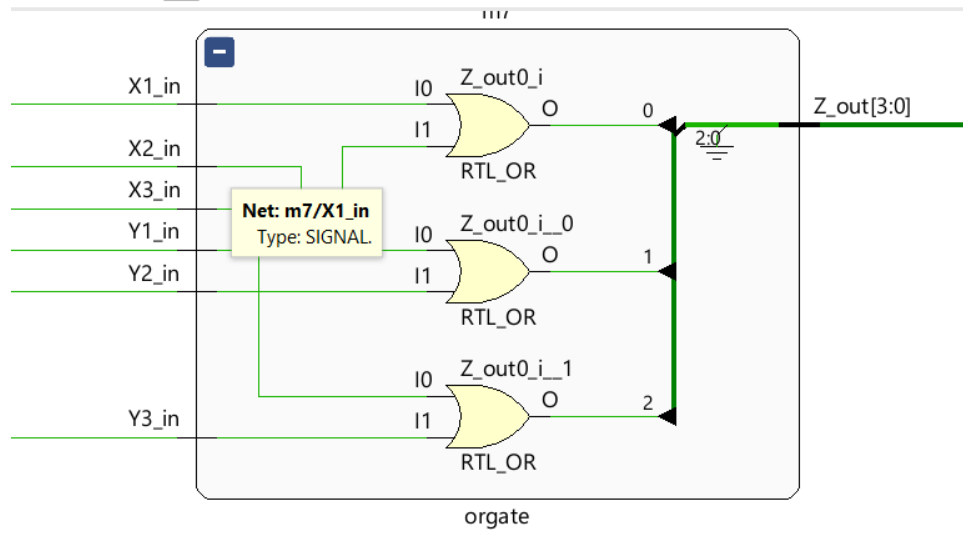


Figure 1.22: RTL Schematic of OR Gate

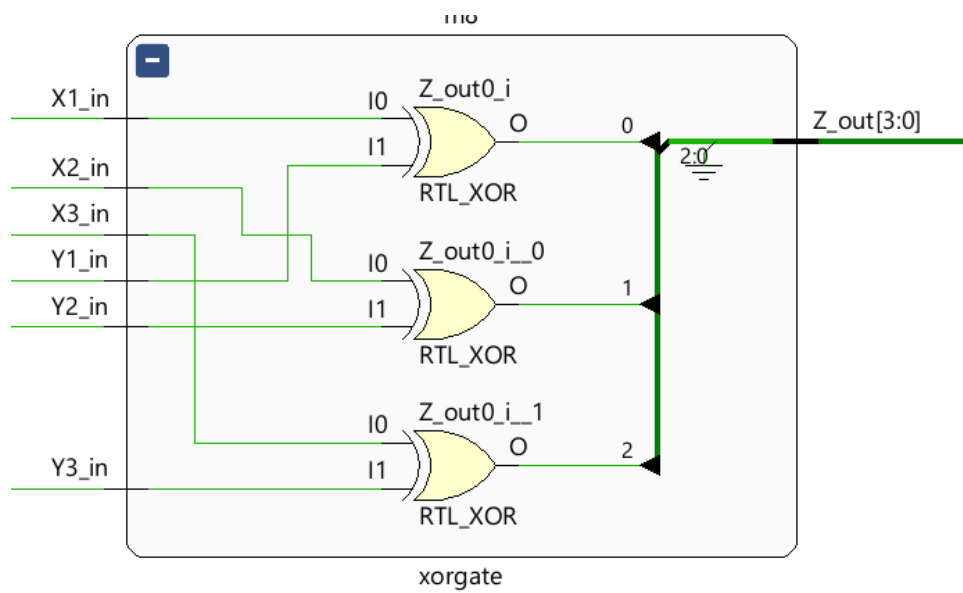


Figure 1.23: RTL Schematic of XOR Gate



## Topmod.vhdl

entity Topmod is

```
Port ( X1_in : in STD_LOGIC;
       X2_in : in STD_LOGIC;
       X3_in : in STD_LOGIC;
       Y1_in : in STD_LOGIC;
       Y2_in : in STD_LOGIC;
       Y3_in : in STD_LOGIC;
       mult : in STD_LOGIC_vector(2 downto 0);
       Z_out : out STD_LOGIC_vector(3 downto 0));
```

end Topmod;

architecture Behavioral of Topmod is

component summation

```
Port ( X1_in : in STD_LOGIC;
       X2_in : in STD_LOGIC;
       X3_in : in STD_LOGIC;
       Y1_in : in STD_LOGIC;
       Y2_in : in STD_LOGIC;
       Y3_in : in STD_LOGIC;
       Z_out : out STD_LOGIC_vector(3 downto 0));
```

end component ;

--subtractor

component subtractor

```
Port ( X1_in : in STD_LOGIC;
       X2_in : in STD_LOGIC;
```

```

        X3_in : in STD_LOGIC;

        Y1_in : in STD_LOGIC;

        Y2_in : in STD_LOGIC;

        Y3_in : in STD_LOGIC;

        Z_out : out std_logic_vector (3 downto 0));
end component;

-- comparator
component comparator
    Port ( X1_in : in STD_LOGIC;

           X2_in : in STD_LOGIC;

           X3_in : in STD_LOGIC;

           Y1_in : in STD_LOGIC;

           Y2_in : in STD_LOGIC;

           Y3_in : in STD_LOGIC;

           Z_out : out std_logic_vector (3 downto 0));
end Component;

-- Rotate left
component Rotateleft
    Port ( X1_in : in STD_LOGIC;

           X2_in : in STD_LOGIC;

           X3_in : in STD_LOGIC;

           Z_out : out std_logic_vector (3 downto 0));
end Component;

-- Onescomplement
component Onescomplement
    Port ( X1_in : in STD_LOGIC;

           X2_in : in STD_LOGIC;

```

```

        X3_in : in STD_LOGIC;

        Z_out : out std_logic_vector (3 downto 0));
end Component;

--Nand gate
component Nandgate
Port ( X1_in : in STD_LOGIC;
        X2_in : in STD_LOGIC;
        X3_in : in STD_LOGIC;
        Y1_in : in STD_LOGIC;
        Y2_in : in STD_LOGIC;
        Y3_in : in STD_LOGIC;
        Z_out : out std_logic_vector (3 downto 0));
end Component;

--orgate
component orgate
Port ( X1_in : in STD_LOGIC;
        X2_in : in STD_LOGIC;
        X3_in : in STD_LOGIC;
        Y1_in : in STD_LOGIC;
        Y2_in : in STD_LOGIC;
        Y3_in : in STD_LOGIC;
        Z_out : out std_logic_vector (3 downto 0));
end Component;

--xorgate
component xorgate
Port ( X1_in : in STD_LOGIC;

```

```

    X2_in : in STD_LOGIC;
    X3_in : in STD_LOGIC;
    Y1_in : in STD_LOGIC;
    Y2_in : in STD_LOGIC;
    Y3_in : in STD_LOGIC;
    Z_out : out std_logic_vector (3 downto 0));
end Component;

signal X1in,x2in,x3in,y1in,y2in,y3in: std_logic;
signal out1, out2,out3,out4,out5,out6,out7,out8: std_logic_vector(3 downto 0);
begin
X1in <= X1_in;
X2in <= X2_in ;
x3in <= X3_in;
y1in <= Y1_in ;
y2in <= y2_in;
y3in <= Y3_in;

m1: summation
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out1);

m2: subtractor
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out2);

```

m3: comparator

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out3);
```

m4: Rotateleft

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Z_out => out4);
```

m5: Onescomplement

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Z_out => out5);
```

m6: Nandgate

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out6);
```

m7: orgate

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out7);
```

m8: xorgate

```
port map(X1_in =>X1in , X2_in => x2in , X3_in => x3in,  
        Y1_in => Y1in, Y2_in =>y2in, Y3_in =>y3in , Z_out => out8);
```

```
process (mult,out1, out2,out3,out4,out5,out6,out7,out8)
```

```
begin
```

```
if mult = "000" then
```

```
Z_out <= out1;
elsif mult = "001" then
Z_out <= out2;
elsif mult = "010" then
Z_out <= out3;
elsif mult = "011" then
Z_out <= out4;
elsif mult = "100" then
Z_out <= out5;
elsif mult = "101" then
Z_out <= out6;
elsif mult = "110" then
Z_out <= out7;
elsif mult = "111" then
Z_out <= out8;
else
Z_out <= "0000";
end if;
end process;
```

end Behavioral;

### **Summation.vhdl**

entity summation is

```
Port ( X1_in : in STD_LOGIC;
```

```
X2_in : in STD_LOGIC;
X3_in : in STD_LOGIC;
Y1_in : in STD_LOGIC;
Y2_in : in STD_LOGIC;
Y3_in : in STD_LOGIC;
Z_out : out STD_LOGIC_vector(3 downto 0));
end summation;
```

architecture Behavioral of summation is

--half adder

component half\_adder

```
Port ( ha_in1 : in STD_LOGIC;
      ha_in2 : in STD_LOGIC;
      has : out STD_LOGIC;
      hac_out : out STD_LOGIC);
```

end component;

--component full\_adder

component full\_adder

```
Port ( fa_in1 : in STD_LOGIC;
      fa_in2 : in STD_LOGIC;
      fa_in3 : in STD_LOGIC;
      fas : out STD_LOGIC;
      fac_out : out STD_LOGIC);
```

end component;

signal hc, fac1: std\_logic;

begin

ha: half\_adder

Port map(ha\_in1=> x1\_in, ha\_in2 => y1\_in, has=>Z\_out(0), hac\_out=> hc);

fa1: full\_adder

Port map(fa\_in1 => hc, fa\_in2 => x2\_in, fa\_in3 => y2\_in, fas => Z\_out(1), fac\_out=>fac1);

fa2: full\_adder

Port map(fa\_in1 => fac1, fa\_in2 => x3\_in, fa\_in3 => y3\_in, fas=> Z\_out(2), fac\_out =>  
Z\_out(3));

end Behavioral;

### **Half adder.vhdl**

entity half\_adder is

Port ( ha\_in1 : in STD\_LOGIC;

ha\_in2 : in STD\_LOGIC;

has : out STD\_LOGIC;

hac\_out : out STD\_LOGIC);

end half\_adder;

architecture Behavioral of half\_adder is

begin

has <= ha\_in1 xor ha\_in2;

hac\_out <= ha\_in1 and ha\_in2;

end Behavioral;



### **Full\_adder.vhdl**

entity full\_adder is

```
__Port ( fa_in1 : in STD_LOGIC;  
____ fa_in2 : in STD_LOGIC;  
____ fa_in3 : in STD_LOGIC;  
____ fas : out STD_LOGIC;  
____ fac_out : out STD_LOGIC);  
end full_adder;
```

architecture Behavioral of full\_adder is

begin

```
fas<= fa_in1 xor fa_in2 xor fa_in3 ;  
fac_out <= (fa_in1 and fa_in2) or (fa_in1 and fa_in3) or (fa_in2 and fa_in3) ;
```

end Behavioral;

### **Subtractor.vhdl**

entity Subtractor is

```
Port ( X1_in : in STD_LOGIC;  
      X2_in : in STD_LOGIC;  
      X3_in : in STD_LOGIC;  
      Y1_in : in STD_LOGIC;  
      Y2_in : in STD_LOGIC;  
      Y3_in : in STD_LOGIC;  
      Z_out : out std_logic_vector (3 downto 0));
```

```
end Subtractor;
```

architecture Behavioral of Subtractor is

```
component Full_adder
```

```
Port ( fa_in1 : in STD_LOGIC;
```

```
      fa_in2 : in STD_LOGIC;
```

```
      fa_in3 : in STD_LOGIC;
```

```
      fas : out STD_LOGIC;
```

```
      fac_out : out STD_LOGIC);
```

```
end component ;
```

```
signal fc1,fc2,s: std_logic;
```

```
begin
```

```
fa1: Full_adder
```

```
port map(fa_in1 => X1_in, fa_in2 => (Y1_in XOR '1'), fa_in3 => '1', fas => Z_out(0), fac_out => fc1);
```

```
fa2: Full_adder
```

```
port map(fa_in1 => X2_in, fa_in2 => (Y2_in Xor '1'), fa_in3 => fc1, fas => Z_out(1), fac_out => fc2);
```

```
fa3: Full_adder
```

```
port map(fa_in1 => X3_in , fa_in2 => (Y3_in XOR '1'), fa_in3 => fc2, fas => Z_out(2), fac_out => s);
```

```
Z_out(3) <='0';
```

```
end Behavioral;
```

### **Comparator.vhdl**

entity Comparator is

```
Port ( X1_in : in STD_LOGIC;
```

```
      X2_in : in STD_LOGIC;
```

```
      X3_in : in STD_LOGIC;
```

```

        Y1_in : in STD_LOGIC;
        Y2_in : in STD_LOGIC;
        Y3_in : in STD_LOGIC;
        Z_out : out STD_LOGIC_VECTOR (3 downto 0));
end Comparator;

```

architecture Behavioral of Comparator is

```

signal a1, a2,a3,gt,lt,eq: std_logic ;

```

```

begin

```

```

a1 <= not (X1_in xor Y1_in);

```

```

a2 <= not (X2_in xor Y2_in);

```

```

a3 <= not (X3_in xor Y3_in );

```

```

eq <= a1 and a2 and a3;

```

```

gt <= (X3_in and (not Y3_in)) or (a3 and X2_in and(not Y2_in)) or (a3 and a2 and (X1_in and (not
Y1_in)));

```

```

lt <= not(eq or gt);

```

```

Z_out (0) <= eq;

```

```

Z_out (1) <= gt;

```

```

Z_out (2) <= lt;

```

```

Z_out(3)<='0';

```

```

end Behavioral;

```

### **Rotateleft.vhdl**

entity RotateLeft is

```

    Port ( X1_in : in STD_LOGIC;

```

```
        X2_in : in STD_LOGIC;
        X3_in : in STD_LOGIC;
        Z_out : out STD_LOGIC_Vector(3 downto 0));
end RotateLeft;
```

architecture Behavioral of RotateLeft is

```
begin
Z_out(0)<= X3_in ;
Z_out(1)<= X1_in ;
Z_out(2)<= X2_in;
Z_out (3) <= '0';
```

```
end Behavioral;
```

### **Onescomplement.vhdl**

entity Onescomplement is

```
    Port ( X1_in : in STD_LOGIC;
           X2_in : in STD_LOGIC;
           X3_in : in STD_LOGIC;
           Z_out : out STD_LOGIC_Vector(3 downto 0));
end Onescomplement;
```

architecture Behavioral of Onescomplement is

```
begin
Z_out(0) <= not X1_in;
Z_out(1) <= not X2_in;
```

```
Z_out(2) <= not X3_in;
```

```
Z_out (3) <= '0';
```

```
end Behavioral;
```

### **Nandgate.vhdl**

```
entity Nandgate is
```

```
Port ( X1_in : in STD_LOGIC;
```

```
      X2_in : in STD_LOGIC;
```

```
      X3_in : in STD_LOGIC;
```

```
      Y1_in : in STD_LOGIC;
```

```
      Y2_in : in STD_LOGIC;
```

```
      Y3_in : in STD_LOGIC;
```

```
      Z_out : out STD_LOGIC_Vector(3 downto 0));
```

```
end Nandgate;
```

```
architecture Behavioral of Nandgate is
```

```
begin
```

```
Z_out(0) <= not (X1_in and Y1_in);
```

```
Z_out(1) <= not (X2_in and Y2_in);
```

```
Z_out(2) <= not (X3_in and Y3_in);
```

```
Z_out (3) <= '0';
```

```
end Behavioral;
```

### orgate.vhdl

entity orgate is

```
Port ( X1_in : in STD_LOGIC;  
      X2_in : in STD_LOGIC;  
      X3_in : in STD_LOGIC;  
      Y1_in : in STD_LOGIC;  
      Y2_in : in STD_LOGIC;  
      Y3_in : in STD_LOGIC;  
      Z_out : out STD_LOGIC_Vector(3 downto 0));
```

end orgate;

architecture Behavioral of orgate is

begin

```
Z_out(0) <= (X1_in or Y1_in);  
Z_out(1) <= (X2_in or Y2_in);  
Z_out(2) <= (X3_in or Y3_in);  
Z_out (3) <= '0';
```

end Behavioral;

### Xorgate.vhdl

entity xorgate is

```
Port ( X1_in : in STD_LOGIC;  
      X2_in : in STD_LOGIC;
```

```
X3_in : in STD_LOGIC;
Y1_in : in STD_LOGIC;
Y2_in : in STD_LOGIC;
Y3_in : in STD_LOGIC;
Z_out : out STD_LOGIC_Vector(3 downto 0));
end xorgate;
```

architecture Behavioral of xorgate is

```
begin
Z_out(0) <= (X1_in xor Y1_in);
Z_out(1) <= (X2_in xor Y2_in);
Z_out(2) <= (X3_in xor Y3_in);
Z_out (3) <= '0';
end Behavioral;
```

### **Test\_bench.vhdl**

entity Test\_Bench is

end Test\_Bench;

architecture Behavioral of Test\_Bench is

component Topmod

```
Port ( X1_in : in STD_LOGIC;
      X2_in : in STD_LOGIC;
      X3_in : in STD_LOGIC;
```

```

    Y1_in : in STD_LOGIC;
    Y2_in : in STD_LOGIC;
    Y3_in : in STD_LOGIC;
    mult : in STD_LOGIC_vector(2 downto 0);
    Z_out : out STD_LOGIC_vector(3 downto 0));
end component;

signal X1_in, X2_in, X3_in, Y1_in, Y2_in, Y3_in: std_logic ;
signal mult: std_logic_vector (2 downto 0);
signal z_out: std_logic_vector (3 downto 0);
begin
a1: Topmod
    port map( X1_in => X1_in, X2_in => X2_in, X3_in => X3_in, Y1_in => Y1_in,
    Y2_in => Y2_in, Y3_in => Y3_in ,mult=> mult ,z_out =>z_out );
Testbench: process
begin
mult <= "000";
X1_in <= '0';
X2_in <= '0';
X3_in <= '0';
Y1_in <= '0';
Y2_in <= '0';
Y3_in <= '0';
wait for 100ns;
mult <= "000";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';

```



```
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "001";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "010";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "011";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
```

```
wait for 100ns;
mult <= "100";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "101";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "110";
X1_in <= '1';
X2_in <= '1';
X3_in <= '1';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "111";
X1_in <= '1';
```

X2\_in <= '1';

X3\_in <= '1';

Y1\_in <= '1';

Y2\_in <= '1';

Y3\_in <= '1';

-----  
wait for 100ns;

mult <= "000";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

Y1\_in <= '1';

Y2\_in <= '1';

Y3\_in <= '0';

wait for 100ns;

mult <= "001";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

Y1\_in <= '1';

Y2\_in <= '1';

Y3\_in <= '0';

wait for 100ns;

mult <= "010";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

```
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '0';
wait for 100ns;
mult <= "011";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '0';
wait for 100ns;
mult <= "100";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '1';
Y3_in <= '0';

wait for 100ns;
mult <= "101";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '1';
```

```
Y3_in <= '0';  
wait for 100ns;  
mult <= "110";  
X1_in <= '0';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '1';  
Y3_in <= '0';  
wait for 100ns;  
mult <= "111";  
X1_in <= '0';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '1';  
Y3_in <= '0';
```

```
-----  
wait for 100ns;  
mult <= "000";  
X1_in <= '1';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '0';  
Y3_in <= '1';  
wait for 100ns;
```

```
mult <= "001";  
X1_in <= '1';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '0';  
Y3_in <= '1';  
wait for 100ns;  
mult <= "010";  
X1_in <= '1';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '0';  
Y3_in <= '1';  
wait for 100ns;  
mult <= "011";  
X1_in <= '1';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '1';  
Y2_in <= '0';  
Y3_in <= '1';  
wait for 100ns;  
mult <= "100";  
X1_in <= '1';  
X2_in <= '1';
```

```
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '0';
Y3_in <= '1';
wait for 100ns;
mult <= "101";
X1_in <= '1';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '0';
Y3_in <= '1';
wait for 100ns;
mult <= "110";
X1_in <= '1';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '0';
Y3_in <= '1';
wait for 100ns;
mult <= "111";
X1_in <= '1';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '1';
Y2_in <= '0';
```

Y3\_in <= '1';

wait for 100ns;

-----

wait for 100ns;

mult <= "000";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

Y1\_in <= '0';

Y2\_in <= '1';

Y3\_in <= '1';

wait for 100ns;

mult <= "001";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

Y1\_in <= '0';

Y2\_in <= '1';

Y3\_in <= '1';

wait for 100ns;

mult <= "010";

X1\_in <= '0';

X2\_in <= '1';

X3\_in <= '0';

Y1\_in <= '0';

Y2\_in <= '1';

Y3\_in <= '1';



```
wait for 100ns;
mult <= "011";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '0';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "100";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '0';
Y2_in <= '1';
Y3_in <= '1';

wait for 100ns;
mult <= "101";
X1_in <= '0';
X2_in <= '1';
X3_in <= '0';
Y1_in <= '0';
Y2_in <= '1';
Y3_in <= '1';
wait for 100ns;
mult <= "110";
```

```
X1_in <= '0';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '0';  
Y2_in <= '1';  
Y3_in <= '1';  
wait for 100ns;  
mult <= "111";  
X1_in <= '0';  
X2_in <= '1';  
X3_in <= '0';  
Y1_in <= '0';  
Y2_in <= '1';  
Y3_in <= '1';  
end process;
```

```
end Behavioral;
```